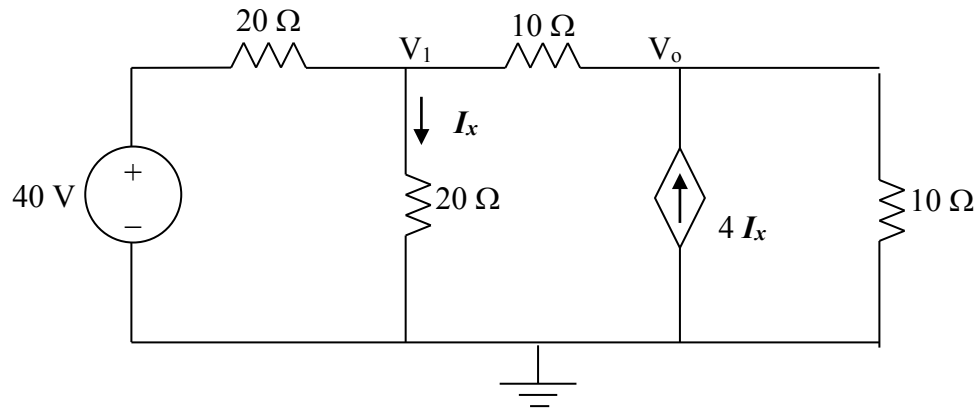


### Solution 3.12

There are two unknown nodes, as shown in the circuit below.



At node 1,

$$\frac{V_1 - 40}{20} + \frac{V_1 - 0}{20} + \frac{V_1 - V_o}{10} = 0 \text{ or}$$

$$(0.05 + 0.05 + 0.1)V_1 - 0.1V_o = 0.2V_1 - 0.1V_o = 2 \quad (1)$$

At node o,

$$\frac{V_o - V_1}{10} - 4I_x + \frac{V_o - 0}{10} = 0 \text{ and } I_x = V_1/20$$

$$-0.1V_1 - 0.2V_1 + 0.2V_o = -0.3V_1 + 0.2V_o = 0 \text{ or} \quad (2)$$


$$V_1 = (2/3)V_o \quad (3)$$

Substituting (3) into (1),

$$0.2(2/3)V_o - 0.1V_o = 0.03333V_o = 2 \text{ or}$$

$$V_o = \mathbf{60 \text{ V}}.$$

### Solution 3.15

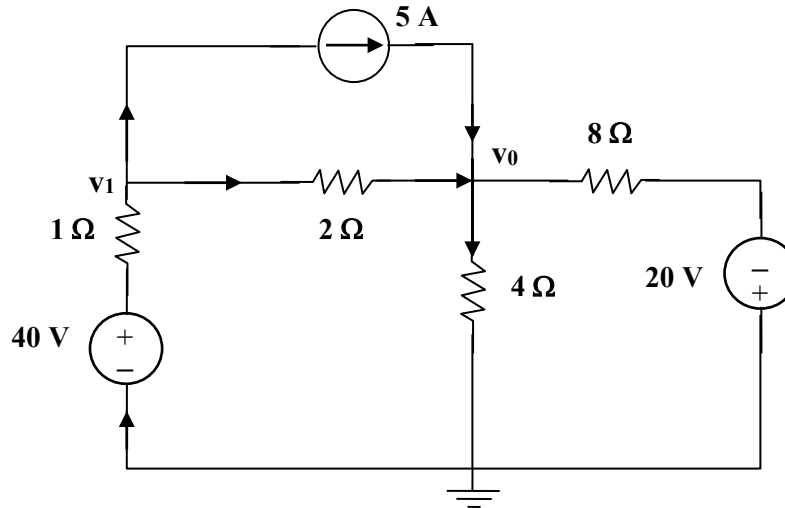

Nodes 1 and 2 form a supernode so that  $v_1 = v_2 + 10$  (1)

At the supernode,  $2 + 6v_1 + 5v_2 = 3(v_3 - v_2) \longrightarrow 2 + 6v_1 + 8v_2 = 3v_3$  (2)

At node 3,  $2 + 4 = 3(v_3 - v_2) \longrightarrow v_3 = v_2 + 2$  (3)

Substituting (1) and (3) into (2),

$$2 + 6v_2 + 60 + 8v_2 = 3v_2 + 6 \longrightarrow v_2 = \frac{-56}{11}$$

$$v_1 = v_2 + 10 = \frac{54}{11}$$


$$i_0 = 6v_1 = \mathbf{29.45 \text{ A}}$$

$$P_{65} = \frac{v_1^2}{R} = v_1^2 G = \left(\frac{54}{11}\right)^2 6 = \mathbf{144.6 \text{ W}}$$

$$P_{55} = v_2^2 G = \left(\frac{-56}{11}\right)^2 5 = \mathbf{129.6 \text{ W}}$$

$$P_{35} = (v_L - v_3)^2 G = (2)^2 3 = \mathbf{12 \text{ W}}$$

**Solution 3.16**

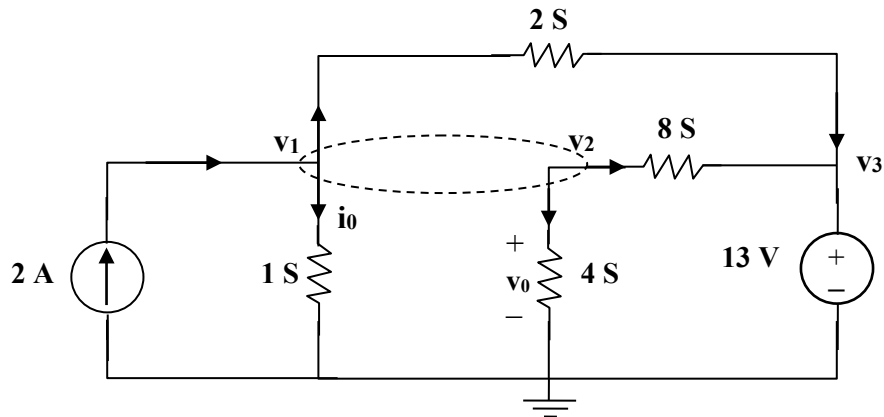

At the supernode,

$$2 = v_1 + 2(v_1 - v_3) + 8(v_2 - v_3) + 4v_2, \text{ which leads to } 2 = 3v_1 + 12v_2 - 10v_3 \quad (1)$$

But

$$v_1 = v_2 + 2v_0 \text{ and } v_0 = v_2.$$

Hence

$$v_1 = 3v_2 \quad (2)$$


$$v_3 = 13V \quad (3)$$

Substituting (2) and (3) with (1) gives,

$$v_1 = 18.858 \text{ V}, v_2 = 6.286 \text{ V}, v_3 = 13 \text{ V}$$
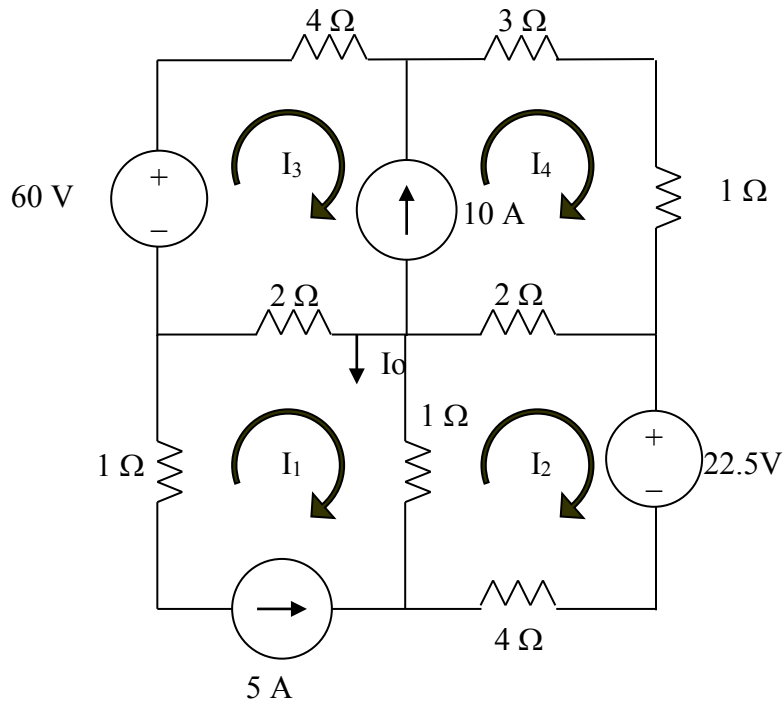
### Solution 3.38

Consider the circuit below with the mesh currents.



$$I_1 = -5 \text{ A} \quad (1)$$

$$\begin{aligned} 1(I_2 - I_1) + 2(I_2 - I_4) + 22.5 + 4I_2 &= 0 \\ 7I_2 - I_4 &= -27.5 \end{aligned} \quad (2)$$

$$\begin{aligned} -60 + 4I_3 + 3I_4 + 1I_4 + 2(I_4 - I_2) + 2(I_3 - I_1) &= 0 \text{ (super mesh)} \\ -2I_2 + 6I_3 + 6I_4 &= +60 - 10 = 50 \end{aligned} \quad (3)$$

But, we need one more equation, so we use the constraint equation  $-I_3 + I_4 = 10$ . This now gives us three equations with three unknowns.

$$\begin{bmatrix} 7 & 0 & -1 \\ -2 & 6 & 6 \\ 0 & -1 & 1 \end{bmatrix} \begin{bmatrix} I_2 \\ I_3 \\ I_4 \end{bmatrix} = \begin{bmatrix} -27.5 \\ 50 \\ 10 \end{bmatrix}$$

We can now use MATLAB to solve the problem.

$$>> Z=[7,0,-1;-2,6,6;0,-1,0]$$

$Z =$

```
    7   0  -1
   -2   6   6
    0  -1   0
>> V=[-27.5,50,10]'
```

$V =$

```
  -27.5
    50
    10
>> I=inv(Z)*V
```

$I =$


```
  -1.3750
 -10.0000
  17.8750
```

$$I_o = I_1 - I_2 = -5 - 1.375 = \mathbf{-6.375 \text{ A.}}$$

Check using the super mesh (equation (3)):

$$-2I_2 + 6 I_3 + 6I_4 = 2.75 - 60 + 107.25 = 50!$$

### Solution 3.45

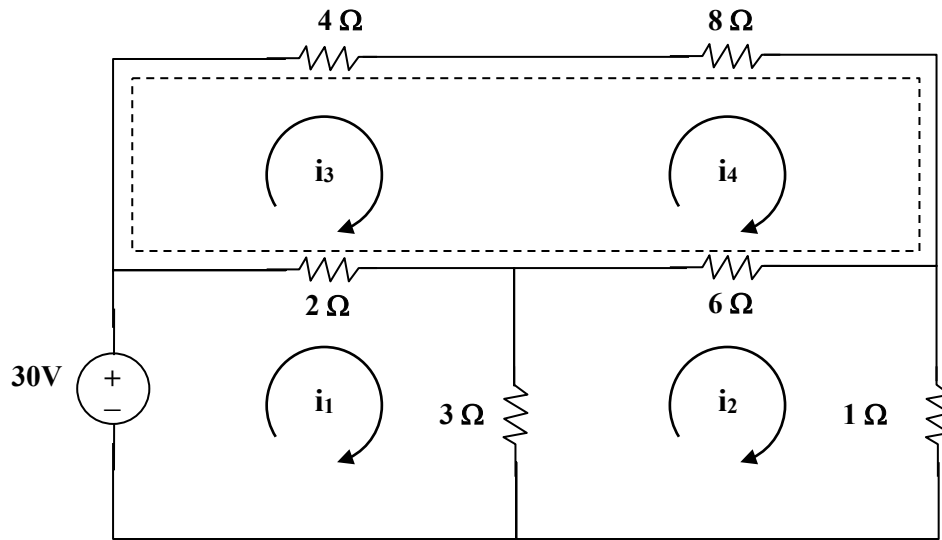

For loop 1,  $30 = 5i_1 - 3i_2 - 2i_3$  (1)


For loop 2,  $10i_2 - 3i_1 - 6i_4 = 0$  (2)

For the supermesh,  $6i_3 + 14i_4 - 2i_1 - 6i_2 = 0$  (3)

But  $i_4 - i_3 = 4$  which leads to  $i_4 = i_3 + 4$  (4)

Solving (1) to (4) by elimination gives  $i = i_1 = \mathbf{8.561\text{ A}}$ .

### Solution 3.52

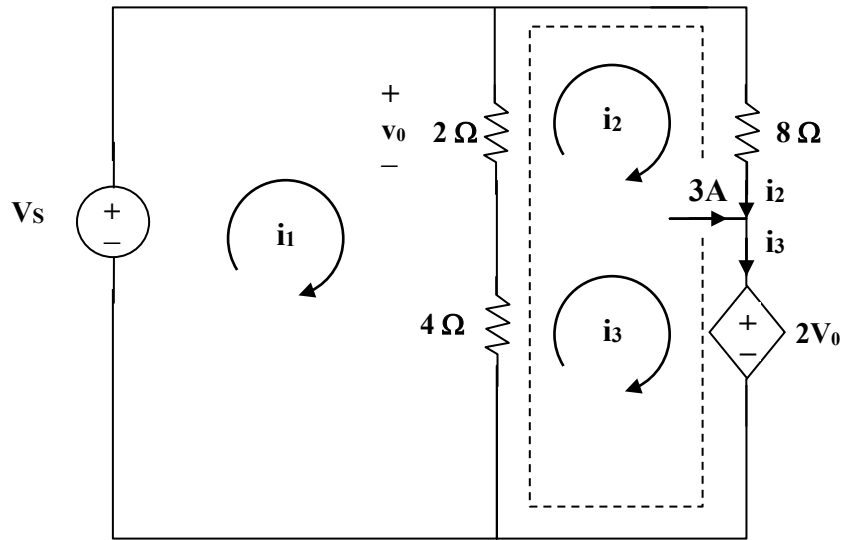

For mesh 1,

$$2(i_1 - i_2) + 4(i_1 - i_3) - 12 = 0 \text{ which leads to } 3i_1 - i_2 - 2i_3 = 6 \quad (1)$$

For the supermesh,  $2(i_2 - i_1) + 8i_2 + 2v_0 + 4(i_3 - i_1) = 0$

But  $v_0 = 2(i_1 - i_2)$  which leads to  $-i_1 + 3i_2 + 2i_3 = 0$   
(2)

For the independent current source,  $i_3 = 3 + i_2$  (3)

Solving (1), (2), and (3), we obtain,

$$i_1 = \mathbf{3.5 \text{ A}}, \quad i_2 = \mathbf{-0.5 \text{ A}}, \quad i_3 = \mathbf{2.5 \text{ A}}.$$